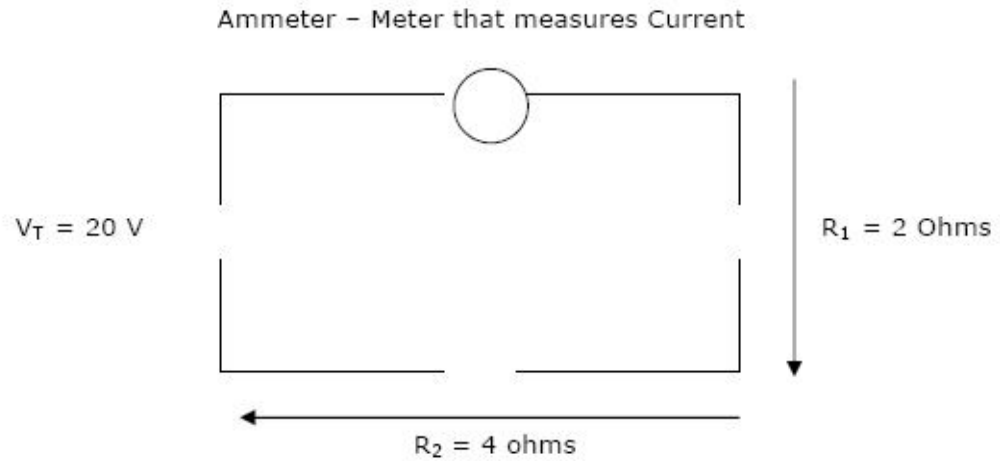


Series and Parallel Circuits Handout

H) Series and Parallel circuits

- 1) **Series circuit** - circuit that has only **one current path**



Reference Table Equations

a) $I_T =$

b) $R_T =$


c)

d) $V_T =$

Find the total current (I_T)

Answer :

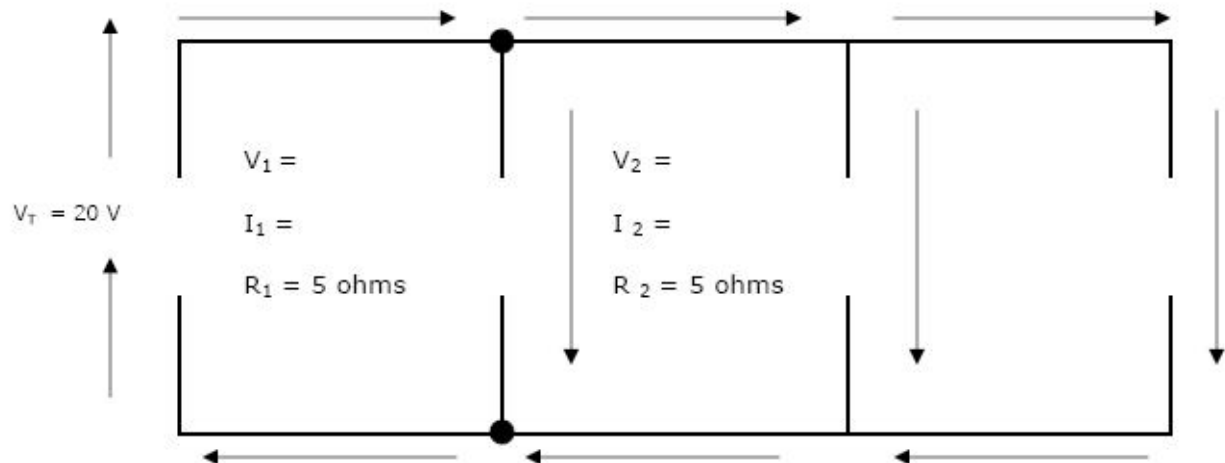2) **Parallel Circuit** - circuit in which each component has its own circular path



a) $I_T =$

For example **If** $I_1 = 2\text{ amps}$, $I_2 = 3\text{ amps}$ $I_3 = 4\text{ amps}$

Then $I_T =$ _____amps

b)

*** Write in the correct voltages in the picture above

c)

*** Use the above equations to find the current going through the first and second resistor

$I_1 =$ _____

$I_2 =$ _____

****If the **total current** in this circuit is **18 amps**, what is the current going through the last resistor?

****What's R_3 ? _____

Finding Total Resistance in a Parallel Circuit

Deriving an Equation for Total Resistance

Since $I_T =$

Then ...

On Reference Table

R_T - total Resistance is also called

-
-
-

Find the total Resistance for three resistors of 2 ohms, 5 ohms and 2 ohms connected in parallel.

1. Substitute

2. Find common denominator and solve